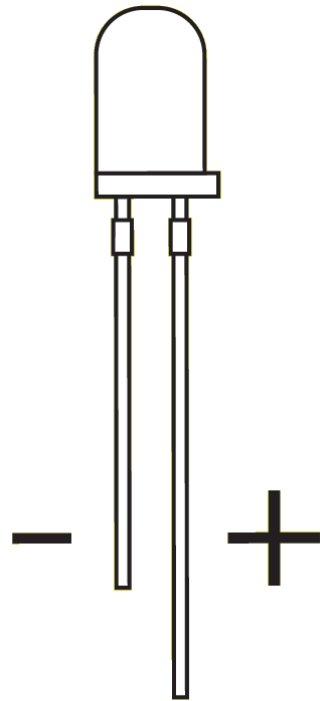


Lighting up the LED!



Taking care of polarity!



Extending the circuit!



Lighting up the LED Card!

